

CSE101 Circuit

Author: ICS Strategy Group

1. Basic logic gates and their truth tables

Inputs		C
A	B	A AND B
0	0	0
0	1	0
1	0	0
1	1	1

Inputs		A OR B
A	B	A OR B
0	0	0
0	1	1
1	0	1
1	1	1

Inputs		A XOR B
A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0

Inputs	NOT A
A	NOT A
0	1
1	0

Fig. 4.2 Basic digital logic gates.

© Pearson Education 2001

可以把 XOR 理解为不等号方便记忆

2. Alternative notations(替代符号)

and: \wedge , **&**

or: \vee

xor: $|$

not: \neg , **-**

3. N~ gate example




NAND gate, $Y = \text{not } (A \text{ and } B)$



NOR gate, $Y = \text{not } (A \text{ or } B)$

4. Selector circuit

 

- This circuit implements the function:

- $Y = \text{not } (V \text{ and } W)$,
- where,
- $V = \text{not } (A \text{ and } S)$,
- $W = \text{not } (Z \text{ and } B)$,
- $Z = \text{not } (S \text{ and } S)$
 $= \text{not } S$.

- Combining altogether we get:

$$Y = \text{not } (\text{not } (A \text{ and } S) \text{ and not } (\text{not } (S) \text{ and } B)).$$

A	B	S	A and S	V	Z	Z and B	W	V and W	Y
0	0	0	0	1	1	0	1	1	0
0	0	1	0	1	0	0	1	1	0
0	1	0	0	1	1	1	0	0	1
0	1	1	0	1	0	0	1	1	0
1	0	0	0	1	1	0	1	1	0
1	0	1	1	0	0	0	1	0	1
1	1	0	0	1	1	1	0	0	1
1	1	1	1	0	0	0	1	0	1

- One may give a short definition of the function from the truth table:

If $S = 1$ then $Y = A$

if $S = 0$ then $Y = B$

Or $Y = (S \& A) \vee (\neg S \& B)$

5. Data selector

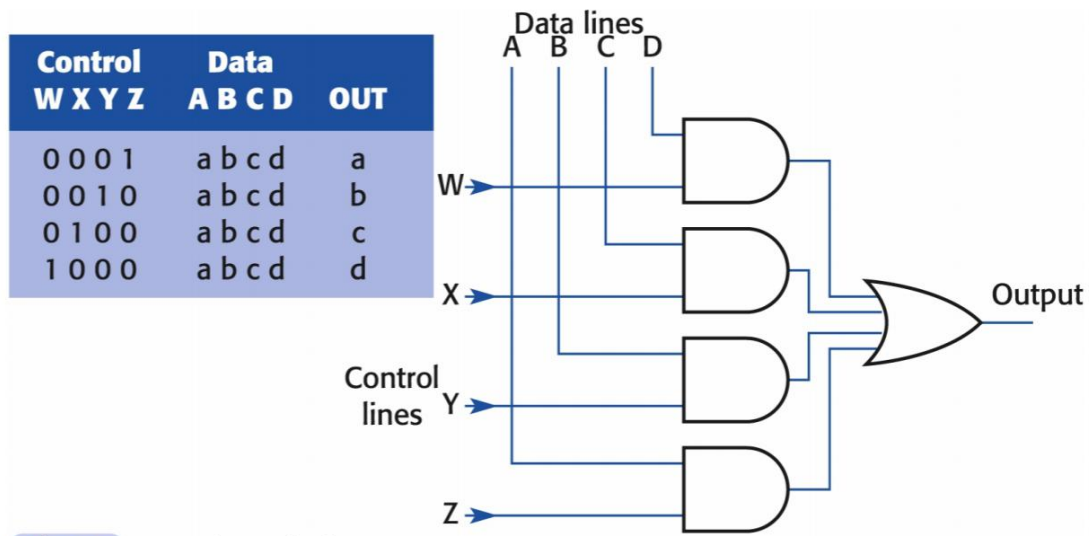


Fig. 4.5 Data selector circuit.

© Pearson Education 2001

6. Two-line decoder

(Very Important, Lecture 23, P7~P14)

Two-line decoder

Selector		Line			
Y	X	d	c	b	a
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Fig. 4.6 A two-line decoder.

© Pearson Education 2001

Data selector with two-line decoder

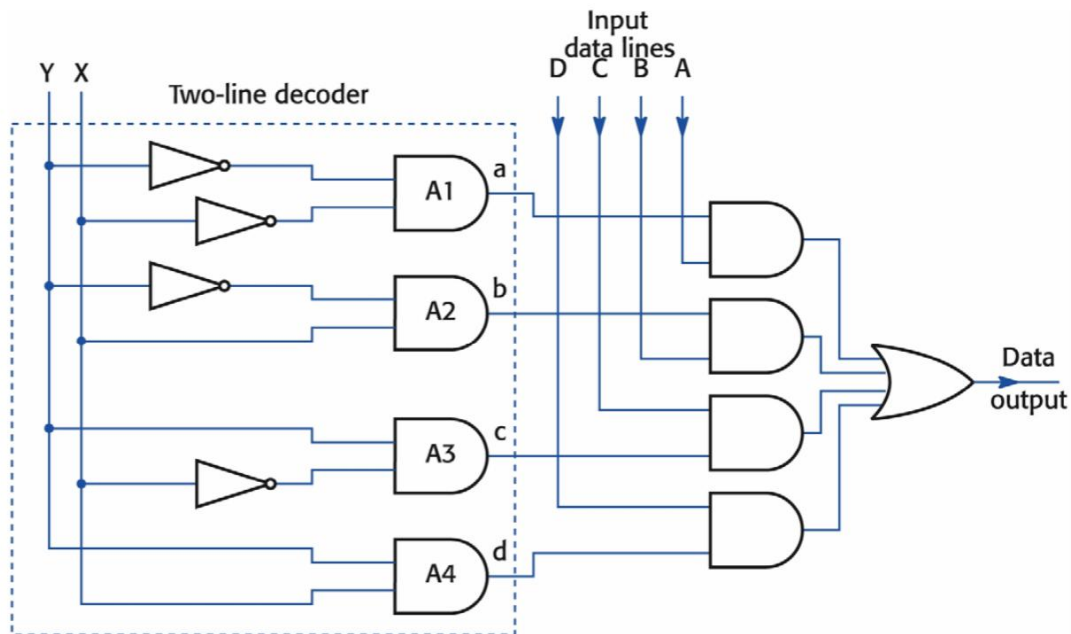


Fig. 4.7 Data multiplexer circuit using a two-line decoder.

© Pearson Education 2001

7. How to design a circuit from a truth table

(Very Important)

Truth Table -> Short form -> Logic Expression -> Implementation

Example:

Truth Table:

Truth table

i_1	i_2	i_3	i_4	O_1
1	1	0	0	1
1	1	0	1	1
0	0	1	0	1
1	0	1	0	1
0	1	0	1	1
.....				0
	...			0
.....				0

Step 1: Get the short form (* means 0 or 1)

Short form

i_1	i_2	i_3	i_4	O_1
1	1	0	*	1
*	0	1	0	1
0	1	0	1	1

Step 2: Get the logic expression

$$O_1 = (i_1 \text{ and } i_2 \text{ and } (\text{not } i_3))$$


or

$$((\text{not } i_2) \text{ and } i_3 \text{ and } (\text{not } i_4))$$

or

$$((\text{not } i_1) \text{ and } i_2 \text{ and } (\text{not } i_3) \text{ and } i_4).$$

Step 3: Implement

 


$$O = (i_1 \text{ and } i_2 \text{ and } (\text{not } i_3)) \text{ or } ((\text{not } i_2) \text{ and } i_3 \text{ and } (\text{not } i_4)) \text{ or } ((\text{not } i_1) \text{ and } i_2 \text{ and } (\text{not } i_3) \text{ and } i_4)$$

Fig. 4.9 Implementing a sum-of-products logic equation.

 8. Half adder

Carry means overflow, Sum means the result

- Binary addition. For the addition of single-bit binary numbers: (Half-)adder.



Other possible designs for half adder

 


Fig. 5.3 Adder v.2.

© Pearson Education 2001



 


Fig. 5.4 Adder v.3.

© Pearson Education 2001

 

个人比较推崇记住这种：

 


因为这样的话可以直接通过上面根据真值表画电

路的方法画出来，只需要把两个输出结果分开做就好了。

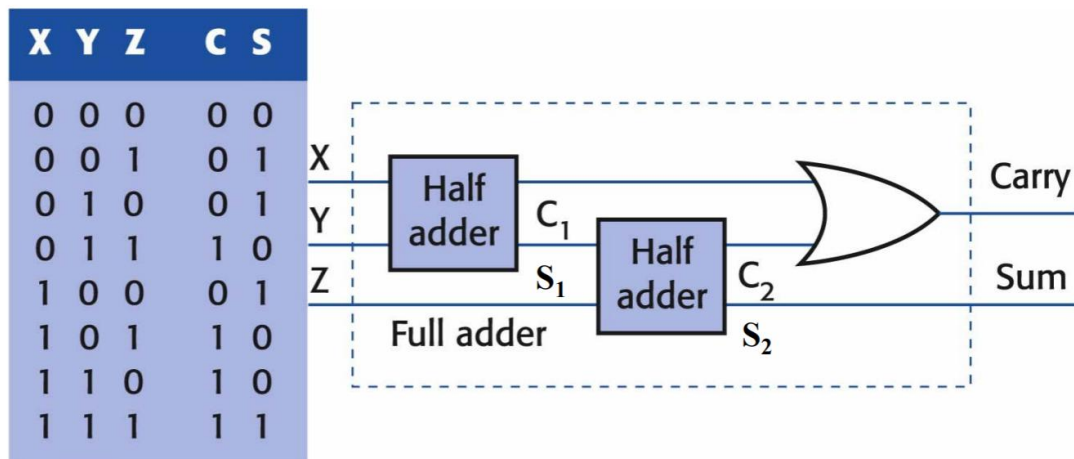9. Full adder

Carry means overflow, Sum means the result

- For the addition of multi-bit binary numbers one needs to deal with carry-in from previous stage, that means the adder should have three inputs.



因为二进制中三个 1 加一起，最多只可能为 11，即最多 overflow 一次，所以两次累加得到的 Carry 用 OR 连接输出。


10. Sequential logic circuits

- **Combinational** (combinatorial) logic circuits.
 - In all Boolean circuits that we have seen so far, the output at any moment depends only on the input at the same moment.
 - **No memory** is there.
- **Sequential** logic circuits.
 - The output depends also on the **state** of the circuit. The state of the circuit is somehow stored within the circuit.
 - There is a **memory** inside.

重点在组合逻辑电路没有记忆区，但数列逻辑电路有记忆区间。

11. SR flip-flop

Has an illegal state.

 

R	S	Q
0	0	?
0	1	0
1	0	1
1	1	Q_{prev}


prev means previous

即：

当(R,S)从(0,1)变成(1,1)结果 Q 仍旧保持 0


当(R,S)从(1,0)变成(1,1)结果 Q 仍旧保持 1

SR representation

 

FlipFlop (SR)

12. Other types of flip-flops

 

T	Q
0	Q_{prev}
1	\bar{Q}_{prev}

D	Q
0	0
1	1

J	K	Q
0	0	Q_{prev}
0	1	0
1	0	1
1	1	\bar{Q}_{prev}

- All these flip-flops have an input marked for **clock**. The new output occurs when the clock is pulsed, i.e. momentarily changed from 1 to 0.
- CLR (clear) and PR (preset) inputs are used to initialise the flip-flop to known value (0 and 1, respectively).

13. D flip-flops

Can copy data from one register to another.

